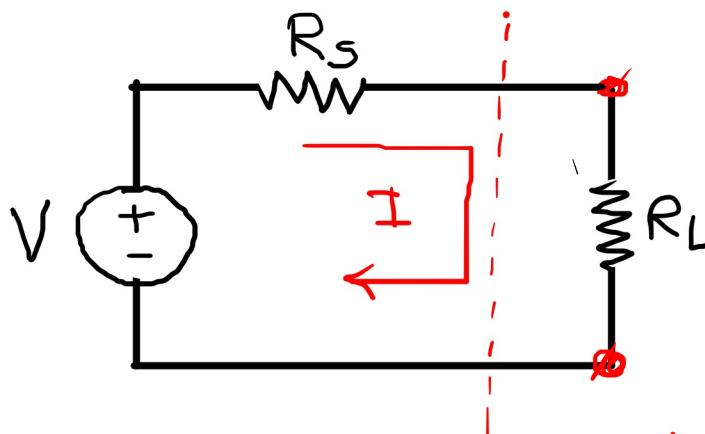


## Maximum Power transfer Theorem

Statement:

The maximum power is delivered from a source to a load when load resistance is equal to source resistance.



$$I = \frac{V}{R_s + R_L} \quad \dots \quad \textcircled{1}$$

Power delivered to load

$$P_L = I^2 R_L = \frac{V^2 \times R_L}{(R_s + R_L)^2}$$

$$\frac{R_L = R_s}{I = \left( \frac{V}{R_s + R_L} \right)}$$

to determine value of  $R_L$  for which maximum power is delivered

$$\frac{dP_L}{dR_L} = 0 \checkmark$$

$$\cdot \frac{dP_L}{dR_L} = \frac{d}{dR_L} \left( \frac{V^2 R_L}{(R_s + R_L)^2} \right) = \frac{V^2 (R_s + R_L)^2 - V^2 R_L \cdot 2(R_s + R_L)}{(R_s + R_L)^4} = 0$$

$$(R_s + R_L)^2 - 2 R_L (R_s + R_L) = 0$$

$$R_s^2 + R_L^2 + 2R_s R_L - 2R_L R_s - 2R_L^2 = 0$$


$$R_s^2 - R_L^2 = 0$$

$\underline{R_s = R_L}$  is condition  
for maximum power transfer

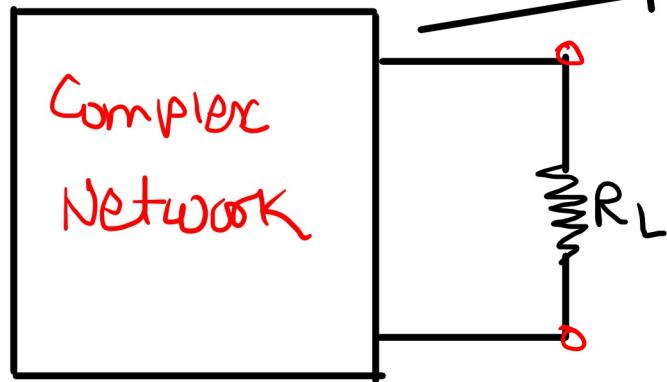
# Maximum Power transfer Theorem

Statement:

The maximum power is delivered from a source to a load when load resistance is equal to source resistance.



Therenvin's  
Equivalent  
circuit

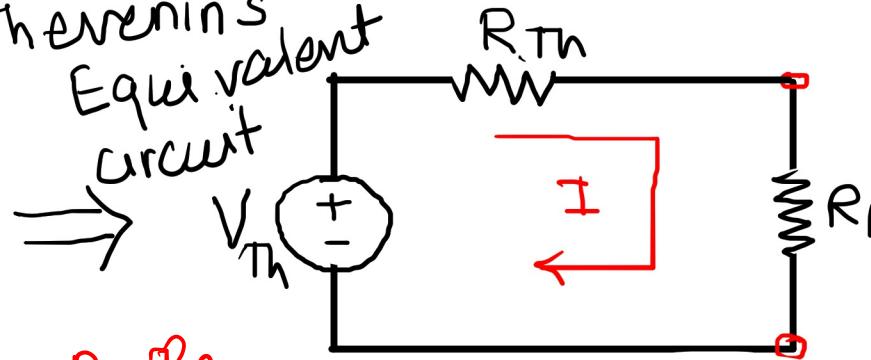

$$V_{RL} = \left( \frac{R_L}{R_L + R_{th}} \right) V_{th}$$

$$I = \frac{V_{th}}{R_L + R_{th}}$$

$$P = I^2 R_L$$


For maximum power  $R_{th} = R_L$

$$P_L = \frac{(V_{th})^2}{(R_L + R_{th})^2} \times R_L \quad \text{OR}$$

$$P_{max} = \frac{(V_{th})^2}{(R_{th} + R_{th})^2} \times R_{th}$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}^2} \times R_{th}$$
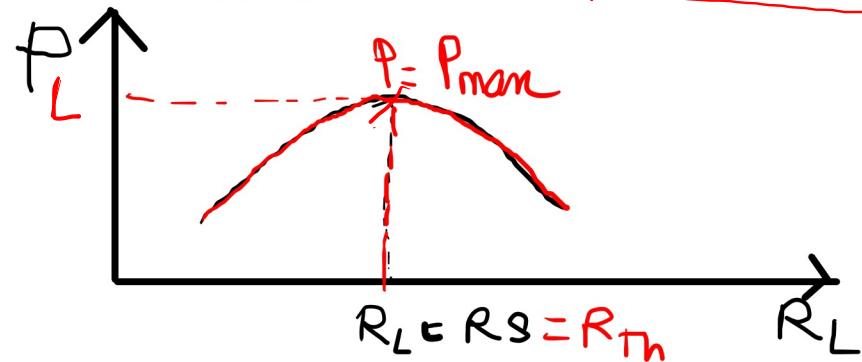
$$\boxed{P_{max} = \frac{(V_{th})^2}{4R_{th}}}$$




$$P_{max} = \frac{(V_{th})^2}{4R_{th}}$$

Steps:

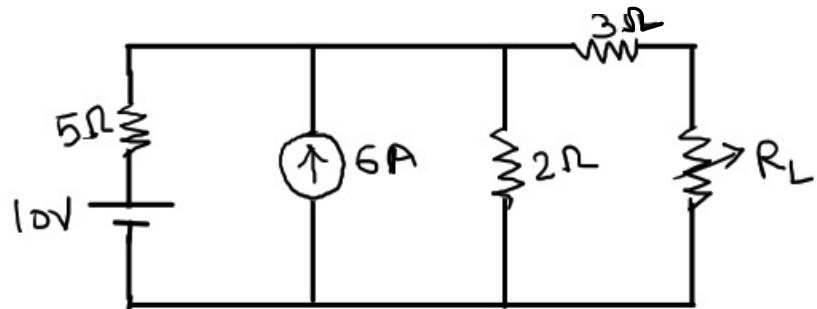
1. Remove Load ✓
2. Find Open circuit Voltage  $V_{th}$  ✓
3. Find  $R_{th}$  ✓
4. Find  $R_L$  for Maximum power transfer ( $R_L=R_{th}$ ) ✓
5. Find Maximum Power

Ex. Find  $R_L$  for maximum power transfer & find maximum power.



$\Rightarrow$  Remove Load  $R_L$   
 $\Rightarrow$  To find  $R_{Th}$

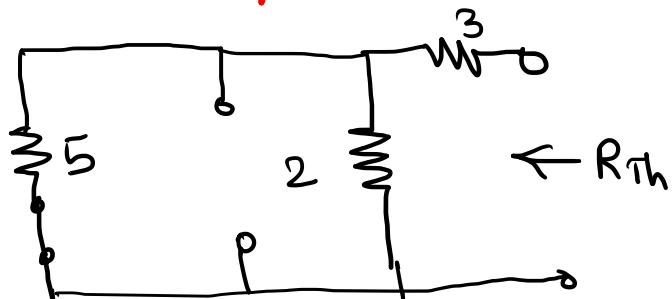$R_L = R_{Th}$  for  
 maximum power transfer




$$R_{Th} = (5||2) + 3 = \frac{10}{7} + 3 =$$

$$R_L = R_{Th} = 4.42\Omega$$

$$\Rightarrow P_{Lmax} = \frac{(V_{Th})^2}{4R_{Th}}$$

$\Rightarrow$  Find  $V_{Th}$

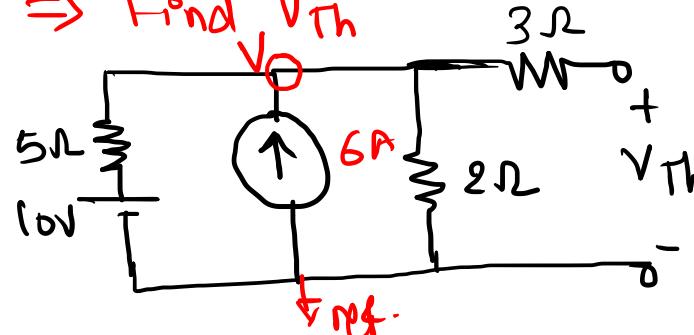

$$V_{Th} = V_{3\Omega} = V_{2\Omega} = V$$

Using Nodal Analysis

$$\frac{V-10}{5} + \frac{V}{2} = 6$$

$$2V - 20 + 5V = 6 \times 10 \\ \Rightarrow V = 80$$

$$V_{Th} = V = \frac{80}{7} = 11.4V$$

$$P_{Lmax} = \frac{(11.4)^2}{4 \times 4.42}$$


$$P_{Lmax} = \frac{(11.4)^2}{17.68}$$

$$P_{Lmax} = 7.35 \text{ Watts}$$

⇒ Find  $R_L$  for maximum power transfer. Also find maximum power.



⇒ Remove  $R_L$  & find  $R_{Th}/V_{Th}$

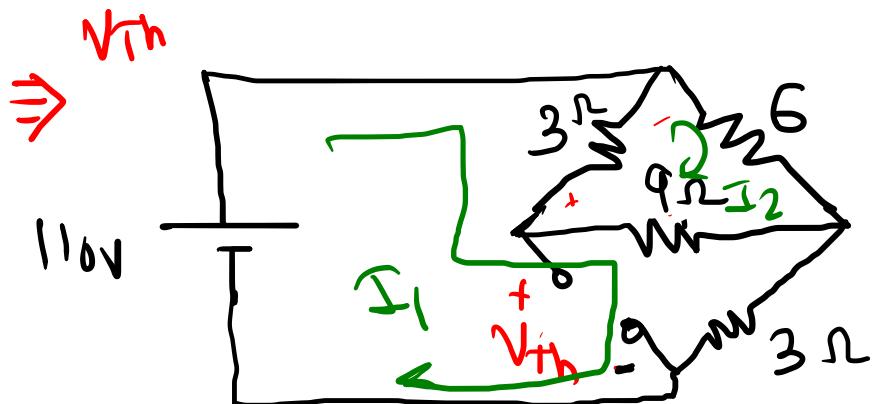

$$V_{Th} - V_{g\Omega} - V_{3\Omega} = 0$$

$$V_{Th} = V_{g\Omega} + V_{3\Omega} \quad \checkmark$$

OR

$$V_{Th} - V_{3\Omega} - 110 = 0$$

$$V_{Th} = V_{3\Omega} + 110$$

KVL to mesh I

$$110 - 3(I_1 - I_2) - 9(I_1 - I_2) - 3I_1 = 0$$

$$110 - 3I_1 + 3I_2 - 9I_1 + 9I_2 - 3I_1 = 0$$

$$15I_1 - 12I_2 = 110 \quad \dots \textcircled{1}$$

KVL to mesh II

$$-3(I_2 - I_1) - 6I_2 - 9(I_2 - I_1) = 0$$

$$12I_1 - 18I_2 = 0 \quad \dots \textcircled{2}$$

Solving \textcircled{1} & \textcircled{2}

$$I_1 = 15.76 \text{ A}, I_2 = 10.47 \text{ A}$$

$$V_{g\Omega} = 9(I_1 - I_2) = 9(15.76 - 10.47)$$

$$V_{g\Omega} = 67.61 \text{ V}$$

$$V_{3\Omega} = 3 \times I_1 = 3 \times 15.76 = 47.28 \text{ V}$$

$$V_{Th} = 67.61 + 47.28 = 94.89 \text{ V}$$


OR

$$V_{Th} = 3(I_2 - I_1) + 110$$

$$= 3(10.47 - 15.71) + 110$$

$$V_{Th} = 94.28 \text{ V}$$

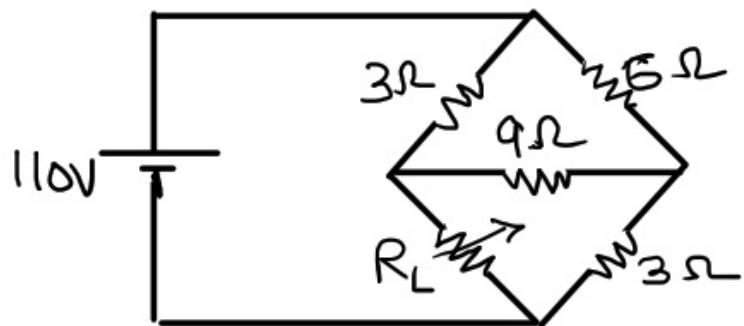⇒ Find  $R_L$  for maximum power transfer. Also find maximum power.





DATA - STAR

$$R_1 = \frac{3 \times 6}{18} = \frac{18}{18} = 1\Omega$$

$$R_2 = \frac{9 \times 6}{18} = 3\Omega$$

$$R_3 = \frac{3 \times 9}{18} = \frac{27}{18} = \frac{3}{2} = 1.5\Omega$$

⇒ Remove  $R_L$  & find  $R_{Th}$

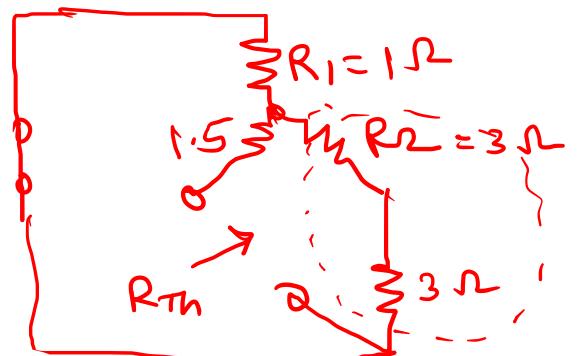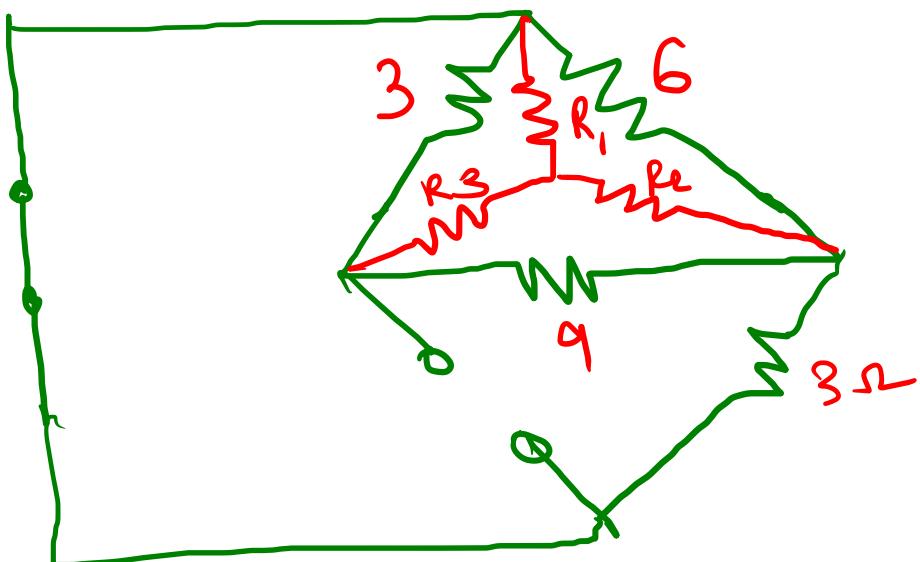

$$R_{Th} = 1.5 + (6 || 1)$$

$$R_{Th} = 1.5 + \frac{6}{7}$$


$$R_{Th} = 1.5 + 0.85$$

$$R_{Th} = 2.35\Omega$$

$\Rightarrow$  Find  $R_L$  for maximum power transfer. Also find maximum power.





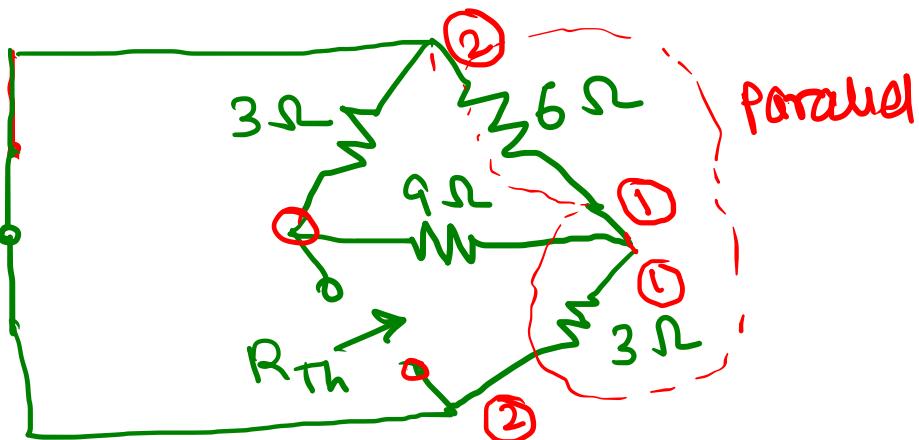$\Rightarrow$  Remove  $R_L$  & find  $R_{Th}$



$$R_L = R_{Th} = \frac{33}{14} = 2.35\Omega$$
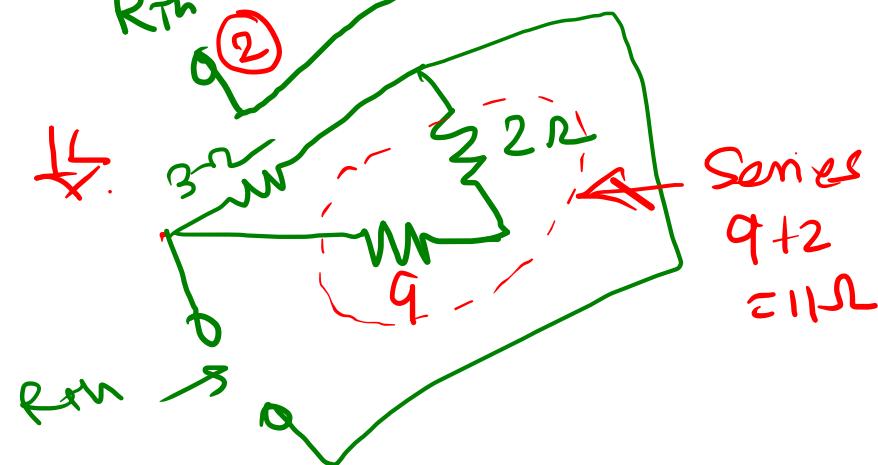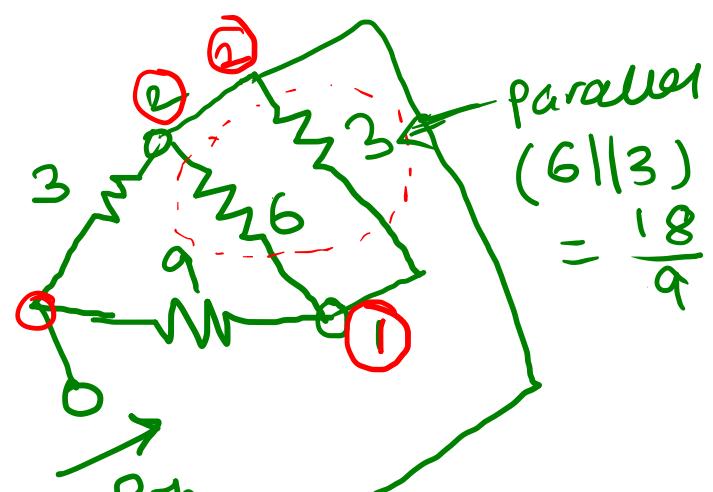
$$P_{L\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(9+28)^2}{4 \times 2.35} = 945 \text{ Watts}$$



$$R_{Th} = 3 \parallel (9+2)$$

$$= 3 \parallel 11 = \frac{33}{14} \Omega$$